



INSTITUTO TECNOLÓGICO DE AERONÁUTICA
DIVISÃO DE CIÊNCIA DA COMPUTAÇÃO - IEC
DEPARTAMENTO DE SISTEMAS DE COMPUTAÇÃO - IEC-SC

EEA-25 - SISTEMAS DIGITAIS PROGRAMÁVEIS

LISTA DE EXERCÍCIOS Nº 8

PROF. ANDRÉ DA FONTOURA PONCHET

SÃO JOSÉ DOS CAMPOS - SP

6 DE NOVEMBRO DE 2023

SUMÁRIO

1	MODELING FINITE-STATE MACHINES IN VERILOG (10,0)	2
1.1	Vending Machine Controller	2

1 MODELING FINITE-STATE MACHINES IN VERILOG (10,0)

1.1 VENDING MACHINE CONTROLLER

Consider the system diagram shown in Figure 1:

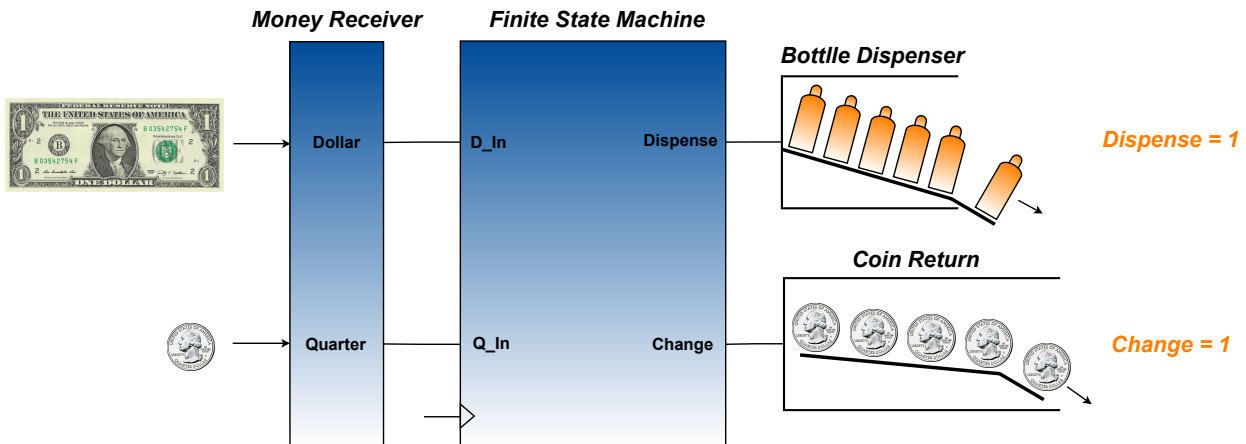


Figura 1: Vending Machine Controller.

You are going to design a simple vending machine controller. The vending machine will sell bottles of water for 75 cents. Customers can enter either a dollar bill or quarters. Once a sufficient amount of money is entered, the vending machine will dispense a bottle of water. If the user entered a dollar, it will return one quarter in change. A **Money Receiver** detects when money has been entered.

The receiver sends two logic signals to our circuit indicating whether the a dollar bill or quarter was received. A **Bottle Dispenser** system holds the water bottles and will release one bottle when its input signal is asserted. A **Coin Return** system holds quarters for change and will release one quarter when its input signal is asserted. The money receiver will reject money if a dollar and quarter are entered simultaneously or if a dollar is entered once the user has started entering quarters.

Follow the examples on pages 252, 253 and 254 from Brock J. LaMer's book (Introduction to Logic Circuits & Logic Design with Verilog) to design the vending machine controller. Design the Verilog Model of the vending machine controller. You can use the code on Example 9.15, page 337, as a reference.

You must show your code and the simulation waveforms in GTKWave.