



EEA-25 Programmable Digital Systems
Prof. André F. Ponchet
Teaching assistant: Felipe Ferreira

Laboratory 03

Last document update: August 21, 2023

1 Objectives

1.1 General Objectives

- Familiarize yourself with the Lattice iCE40 development environment;
- Understand circuit design process using HDLs and FPGA implementation;
- Simulate and verify results with real FPGA boards.

1.2 Specific Objectives

- Implement a digital comparator;
- Exercise the design process seen on the last laboratory;
- Describe a circuit through continuous expressions in Verilog;
- Build a 4-bit comparator and complete the challenge.

2 Lab Development

2.1 Circuit analysis

A digital comparator is a combinational circuit that compares two binary or digital values and determines which one is greater/lesser than the other or if they are equal. The circuit has two inputs: A and B, and three outputs, accordingly to each conditions: $A < B$, $A > B$ and $A = B$.

2.2 HDL coding and simulation

1. Create a folder named "LAB-3";
2. Implement the following code in Verilog, named "magnitude_comparator.v":

```
1 module magnitude_comparator (  
2     // Inputs  
3     input [3:0] a, b,  
4     // Outputs  
5     output aeqb, agtb, altb  
6 );  
7     assign aeqb = (a == b) ? 1'b1 : 1'b0;  
8     assign agtb = (a > b) ? 1'b1 : 1'b0;  
9     assign altb = (a < b) ? 1'b1 : 1'b0;  
10 endmodule
```

3. Create the following testbench code "magnitude_comparator_tb.v" inside the folder, remember to map each port respecting the Unit Under Test (UUT) order:

```

1 'include "magnitude_comparator.v"
2
3 module magnitude_comparator_tb;
4
5     // Inputs
6     reg [3:0] data_a;
7     reg [3:0] data_b;
8
9     // Outputs
10    wire aeqb, agtb, altb;
11
12    // Instantiate the Unit Under Test (UUT)
13    magnitude_comparator uut (data_a, data_b, aeqb, agtb, altb);
14
15    initial begin
16        $dumpfile ("magnitude_comparator_tb.vcd");
17        $dumpvars (0, magnitude_comparator_tb);
18    end
19
20    initial
21        $monitor ($time, " data_a = %d, data_b = %d,
22                    aeqb = %b, agtb = %b, altb = %b",
23                    data_a, data_b, aeqb, agtb, altb);
24
25    initial begin
26        data_a = 4; data_b = 3; #1
27        data_a = 1; data_b = 1; #1
28        data_a = 3; data_b = 4; #1
29        data_a = 10; data_b = 10; #1
30        data_a = 12; data_b = 10; #1;
31        $finish;
32    end
33 endmodule


```

4. Enter the following commands using Linux terminal and open the file "magnitude_comparator_tb.vcd" with **gtkwave**. Compare the results with the following image.

```

1 iverilog magnitude_comparator_tb.v
2 vvp a.out
3 gtkwave magnitude_comparator_tb.vcd

```

 


Comparator simulation.

3 Challenge

- Now that you have been induced to validate the circuit's behavior using ternary operators, we will explore other possibilities to describe it.
- Exploring the concepts seen in digital circuits, we are able to get the logic expression that represents a digital circuit or get a digital circuit from a logic expression, right?
- It is essential to interpret the logic expressions of a circuit to synthesize it or obtain a circuit through its HDL equivalent.

- Your challenge will be to be able to put these concepts into practice!
- The image below represents the circuit responsible for the function $A == B$.

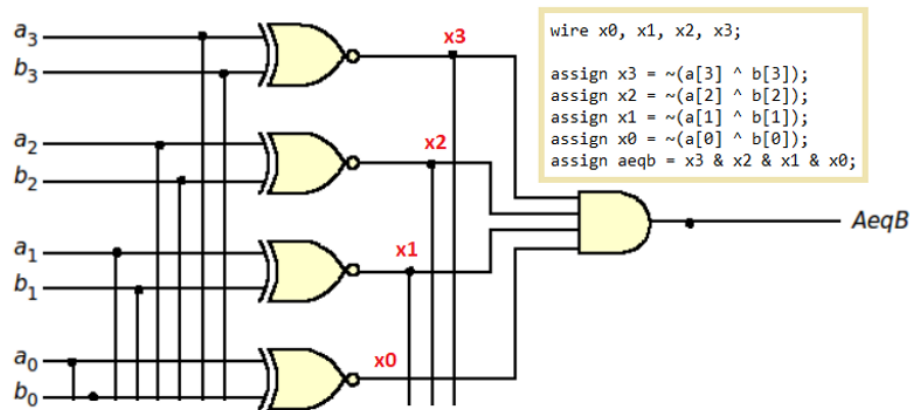

Incomplete 4-bit comparator.

```

1 module magnitude_comparator (
2
3     // Inputs
4     input [3:0] a, b,
5
6     // Outputs
7     output aeqb, agtb, altb
8 );
9     wire x0, x1, x2, x3;
10
11     assign x3 = ~(a[3] ^ b[3]);
12     assign x2 = ~(a[2] ^ b[2]);
13     assign x1 = ~(a[1] ^ b[1]);
14     assign x0 = ~(a[0] ^ b[0]);
15
16     assign aeqb = x3 & x2 & x1 & x0;
17
18     assign agtb = (a > b) ? 1'b1 : 1'b0;
19     assign altb = (a < b) ? 1'b1 : 1'b0;
20 endmodule


```

- Notice that we modified our Verilog file to match the equivalent logic function of the circuit.
- Your challenge in this lab will be to continue the remaining HDL to get the parts responsible for $A > B$ and $A < B$, based on the example above.
- Get the equivalent expression that matches the AgtB output, i.e, $A > B$.

```

1 module magnitude_comparator (
2
3     // Inputs
4     input [3:0] a, b,
5
6     // Outputs
7     output aeqb, agtb, altb
8 );
9     wire x0, x1, x2, x3;
10
11     assign x3 = ~(a[3] ^ b[3]);

```

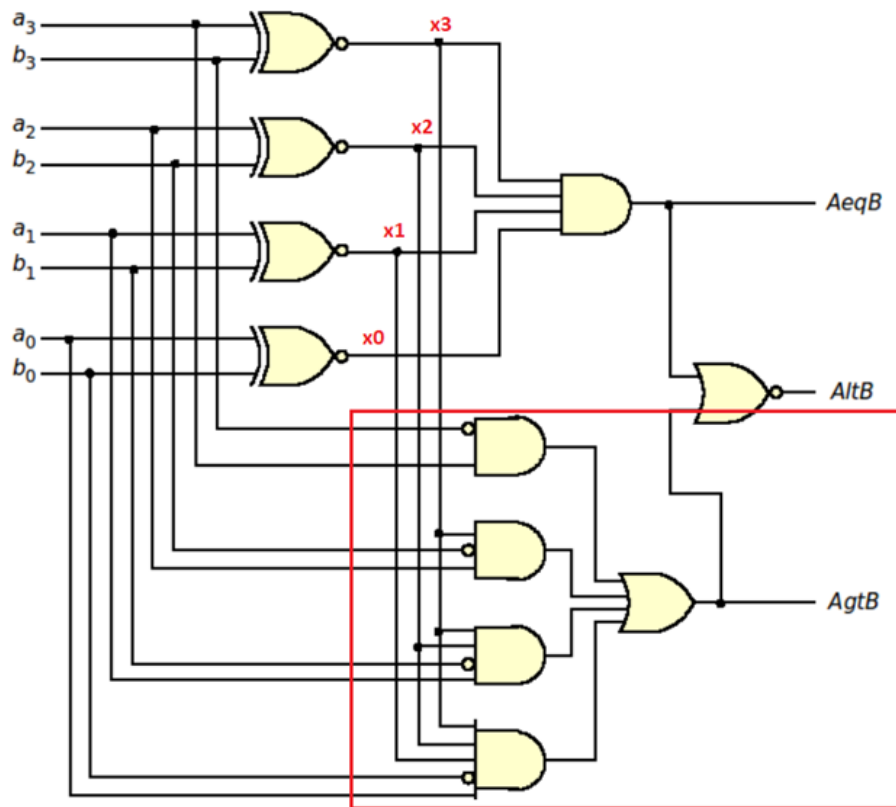

Challenge comparator schematic $A > B$.

```


12  assign x2 = ~(a[2] ^ b[2]);
13  assign x1 = ~(a[1] ^ b[1]);
14  assign x0 = ~(a[0] ^ b[0]);
15
16  assign aeqb = x3 & x2 & x1 & x0;
17
18  assign agtb = a[3]&(~b[3]) | (...)
19  (...)
20 endmodule

```

- The snippet above corresponds to the beginning of the expression you should get, try to complete it.
- Get the equivalent expression that matches the AltB output, i.e, $A < B$.
- Note that you can use the previous expressions as a resource.

4 Exercises

- What differences did you observe between using the data flow approach (functional or logical) and the structural approach?
- Implement the missing functions with the proposed challenge and simulate the circuit using the testbench already provided.
- Propose the description that represents the 4x1 multiplexer circuit below and create a testbench to validate your circuit.
- Desirable: Use data flow approach (logical description).

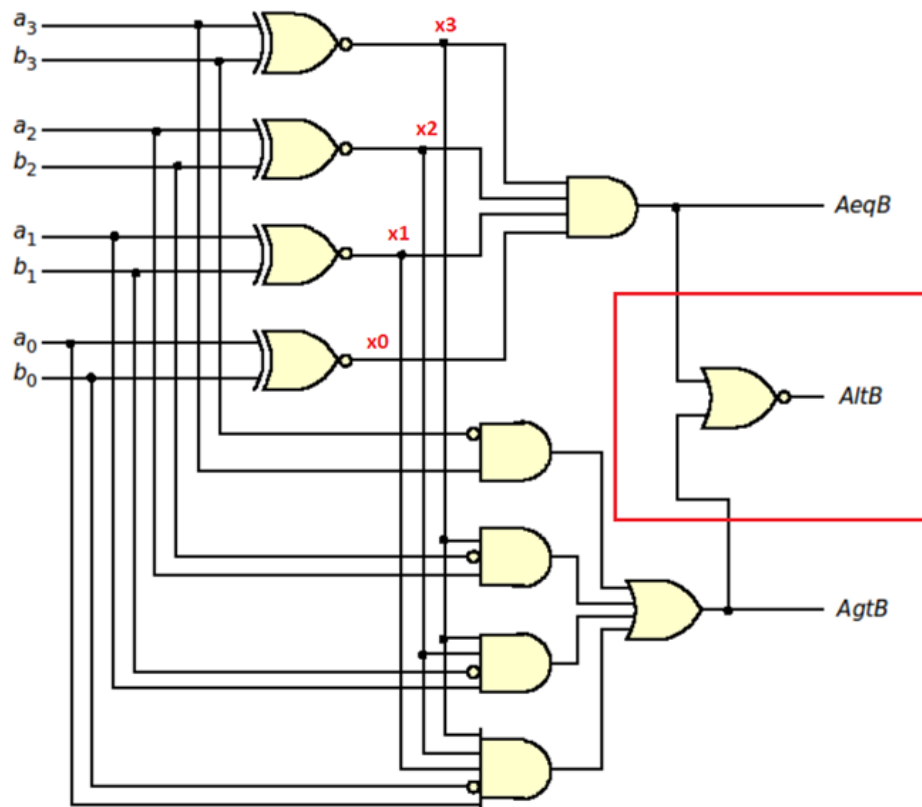

Challenge comparator schematic $A < B$.


```

1 'include "mux_4_1_logic.v"
2 'timescale 1ns/1ps // time unit / simulation precision
3
4 module mux_4_1_tb;
5
6     reg [3:0] IN;
7     reg [1:0] S;
8     reg EN;
9     wire Y;
10
11     mux_4_1_logic uut (EN, IN, S, Y);
12
13     initial begin
14         $dumpfile("mux_4_1_tb.vcd");
15         $dumpvars(0, mux_4_1_tb);
16     end
17
18     initial begin
19
20     end
21
22 endmodule

```

5 Grading

 This lab does not require a report. When finishing it, make sure you enter the line for a direct assessment conducted by the professors or TAs during lab timeframe.



4x1 multiplexer.