



Instituto Tecnológico de Aeronáutica
Departamento de Eletrônica

EEA25 - Prova 1

Daniel Araujo Cavassani

Prof. André da Fontoura Ponchet
São José dos Campos, São Paulo, 22/09/2023

1. Alarm System

a. Tabela Verdade + Equação Lógica

Q1)


a)

S2	S1	S0	A
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		S2S1			
		00	01	11	10
S0	0	0	0	1	0
	1	0	1	1	1

$$A = S2.S1 + S2.S0 + S1.S0$$

b. Circuito

 

c. Código Verilog

CÓDIGO DA LÓGICA:

```
module AlarmSystem(
    input S0,
    input S1,
    input S2,
    output A
);

    wire and1, and2, and3;

    // AND gates
    and(and1, S0, S1);
    and(and2, S1, S2);
    and(and3, S0, S2);

    // OR gate
    or(A, and1, and2, and3);

endmodule
```

2. Patrol System


a. Tabela Verdade + Equação Lógica

a)

S2	S1	S0	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$$P = \overline{S2} \cdot \overline{S1} \cdot S0 + \overline{S2} \cdot S1 \cdot \overline{S0} + S2 \cdot \overline{S1} \cdot \overline{S0}$$

b. Circuito

 

c. Código Verilog

CÓDIGO DA LÓGICA:

```
module PatrolSystem(  
    input S0,  
    input S1,  
    input S2,  
    output P  
);  
    wire and1, and2, and3;  
    wire notS0, notS1, notS2;  
  
    // NOT  
    not(notS0, S0);  
    not(notS1, S1);  
    not(notS2, S2);  
  
    // AND  
    and(and1, notS0, notS1, S2);  
    and(and2, notS0, S1, notS2);  
    and(and3, S0, notS1, notS2);  
  
    // OR  
    or(P, and1, and2, and3);  
endmodule
```

3. Simplified Circuit

a. Equação Simplificada


Q3/

a) Mapa de Karnaugh:

<u>S</u>		$X_4 X_3$			
		$X_2 X_1$	00	01	11
	00	1	1	0	0
	01	0	1	0	1
	11	0	0	0	0
	10	1	1	0	1

$$\sim S = \overline{X_4} \cdot \overline{X_1} + \overline{X_4} \cdot X_3 \cdot \overline{X_2} + \overline{X_3} \cdot X_2 \cdot \overline{X_1} + X_4 \cdot \overline{X_3} \cdot \overline{X_2} \cdot X_1$$

b. Circuito

 

c. Código Verilog

CÓDIGO DA LÓGICA:

```
module SimplifiedCircuit(  
    input X1,  
    input X2,  
    input X3,  
    input X4,  
    output S  
);  
  
    wire and1, and2, and3, and4;  
    wire notX1, notX2, notX3, notX4;  
  
    // NOT  
    not(notX1, X1);  
    not(notX2, X2);  
    not(notX3, X3);  
    not(notX4, X4);  
  
    // AND  
    and(and1, notX4, notX1);  
    and(and2, notX4, X3, notX2);  
    and(and3, notX3, X2, notX1);  
    and(and4, X4, notX3, notX2, X1);  
  
    // OR  
    or(S, and1, and2, and3, and4);  
  
endmodule
```

d. Código Test Verilog + Sinais no GtkWave

CÓDIGO DO TESTBENCH:

```
`include "q3c_SimplifiedCircuit.v"  
`timescale 1ns/1ps  
  
module SimplifiedCircuit_tb;
```

```

// Inputs
reg X1, X2, X3, X4;

// Outputs
wire S;

SimplifiedCircuit uut (
    .X1(X1),
    .X2(X2),
    .X3(X3),
    .X4(X4),
    .S(S)
);

initial begin
    $dumpfile("q3d_SimplifiedCircuit_tb.vcd");
    $dumpvars(0, SimplifiedCircuit_tb);
end

// Monitor the variables
initial $monitor($time,
    " X1 = %b, X2 = %b, X3 = %b, X4 = %b, S = %b",
    X1, X2, X3, X4, S);

initial begin
    // Testa todas as combinações
    {X4, X3, X2, X1} = 4'b0000; #10;
    {X4, X3, X2, X1} = 4'b0001; #10;
    {X4, X3, X2, X1} = 4'b0010; #10;
    {X4, X3, X2, X1} = 4'b0011; #10;
    {X4, X3, X2, X1} = 4'b0100; #10;
    {X4, X3, X2, X1} = 4'b0101; #10;
    {X4, X3, X2, X1} = 4'b0110; #10;
    {X4, X3, X2, X1} = 4'b0111; #10;
    {X4, X3, X2, X1} = 4'b1000; #10;
    {X4, X3, X2, X1} = 4'b1001; #10;
    {X4, X3, X2, X1} = 4'b1010; #10;
    {X4, X3, X2, X1} = 4'b1011; #10;
    {X4, X3, X2, X1} = 4'b1100; #10;

```

```

        {X4, X3, X2, X1} = 4'b1101; #10;
        {X4, X3, X2, X1} = 4'b1110; #10;
        {X4, X3, X2, X1} = 4'b1111; #10;
    $finish;
end

endmodule

```


OUTPUT:

```

danxc@danxc-popos-a72liv:~/Desktop/EEA25/Provas/P1$ iverilog q3d_SimplifiedCircuit_tb.v
danxc@danxc-popos-a72liv:~/Desktop/EEA25/Provas/P1$ vvp a.out
VCD info: dumpfile q3d_SimplifiedCircuit_tb.vcd opened for output.
  0 X1 = 0, X2 = 0, X3 = 0, X4 = 0, S = 1
 10 X1 = 1, X2 = 0, X3 = 0, X4 = 0, S = 0
 20 X1 = 0, X2 = 1, X3 = 0, X4 = 0, S = 1
 30 X1 = 1, X2 = 1, X3 = 0, X4 = 0, S = 0
 40 X1 = 0, X2 = 0, X3 = 1, X4 = 0, S = 1
 50 X1 = 1, X2 = 0, X3 = 1, X4 = 0, S = 1
 60 X1 = 0, X2 = 1, X3 = 1, X4 = 0, S = 1
 70 X1 = 1, X2 = 1, X3 = 1, X4 = 0, S = 0
 80 X1 = 0, X2 = 0, X3 = 0, X4 = 1, S = 0
 90 X1 = 1, X2 = 0, X3 = 0, X4 = 1, S = 1
100 X1 = 0, X2 = 1, X3 = 0, X4 = 1, S = 1
110 X1 = 1, X2 = 1, X3 = 0, X4 = 1, S = 0
120 X1 = 0, X2 = 0, X3 = 1, X4 = 1, S = 0
130 X1 = 1, X2 = 0, X3 = 1, X4 = 1, S = 0
140 X1 = 0, X2 = 1, X3 = 1, X4 = 1, S = 0
150 X1 = 1, X2 = 1, X3 = 1, X4 = 1, S = 0

```

SINAIS NO GTKWAVE:

 

4. Full Adder

a. Equações Lógicas

Q4

a) De acordo com a Tabela Verdade do Full Adder:

$$\begin{aligned} \leadsto \text{Cout}_i &= a_i \cdot b_i + c_{in,i-1} \cdot (a_i \oplus b_i) \\ \leadsto \text{Sum}_i &= a_i \oplus b_i \oplus c_{in,i-1} \end{aligned}$$

b. Código Verilog (estrutural)

CÓDIGO DA LÓGICA:

```
module FullAdder(  
    input a,      // Entrada a  
    input b,      // Entrada b  
    input cin,    // Carry in  
  
    output s,     // Soma  
    output cout   // Carry out  
);  
  
    // Fios intermediários  
    wire w1, w2, w3;  
  
    // XOR para calcular a XOR entre a e b  
    xor u0 (w1, a, b);  
  
    // XOR para calcular a soma final (sum)  
    xor u1 (s, w1, cin);  
  
    // AND para calcular a parte do carry out com cin e XOR de a e b  
    and u2 (w2, cin, w1);
```



```

        // AND para calcular a parte do carry out com a e b
        and u3 (w3, a, b);

        // OR para calcular o carry out final
        or u4 (cout, w2, w3);

    endmodule

```

c. Código Test Verilog + Sinais no GtkWave

CÓDIGO DO TESTBENCH:

```

`include "q4b_FullAdder.v"
`timescale 1ns/1ps

module FullAdder_tb;

    // Entradas
    reg a;
    reg b;
    reg cin;

    // Saídas
    wire s;
    wire cout;

    // Instanciar o módulo FullAdder
    FullAdder uut (
        .a(a),
        .b(b),
        .cin(cin),
        .s(s),
        .cout(cout)
    );

    initial begin
        $dumpfile("q4c_FullAdder_tb.vcd");
        $dumpvars(0, FullAdder_tb);
    end

```

```

// Monitorar as variáveis
initial $monitor($time,
                " a = %b, b = %b, cin = %b, s = %b, cout = %b",
                a, b, cin, s, cout);

// Testes
initial begin
    // Testar todas as combinações possíveis de a, b e cin
    {cin, b, a} = 3'b000; #10;
    {cin, b, a} = 3'b001; #10;
    {cin, b, a} = 3'b010; #10;
    {cin, b, a} = 3'b011; #10;
    {cin, b, a} = 3'b100; #10;
    {cin, b, a} = 3'b101; #10;
    {cin, b, a} = 3'b110; #10;
    {cin, b, a} = 3'b111; #10;
    $finish;
end

endmodule

```


OUTPUT:

```

danxc@danxc-popos-a72liv:~/Desktop/EEA25/Provas/P1$ iverilog q4c_FullAdder_tb.v
danxc@danxc-popos-a72liv:~/Desktop/EEA25/Provas/P1$ vvp a.out
VCD info: dumpfile q4c_FullAdder_tb.vcd opened for output.
  0 a = 0, b = 0, cin = 0, s = 0, cout = 0
 10 a = 1, b = 0, cin = 0, s = 1, cout = 0
 20 a = 0, b = 1, cin = 0, s = 1, cout = 0
 30 a = 1, b = 1, cin = 0, s = 0, cout = 1
 40 a = 0, b = 0, cin = 1, s = 1, cout = 0
 50 a = 1, b = 0, cin = 1, s = 0, cout = 1
 60 a = 0, b = 1, cin = 1, s = 0, cout = 1
 70 a = 1, b = 1, cin = 1, s = 1, cout = 1

```

SINAIS NO GTKWAVE:

 

5. Clock Divider

CÓDIGO DA LÓGICA:

```
// Módulo do D-flip-flop
module d_flip_flop (
    output reg Q, Qn,
    input wire Clock, Reset, D
);

    // Inicialização dos estados dos flip-flops
    initial begin
        Q = 1'b0;
        Qn = 1'b1;
    end

    always @(posedge Clock or negedge Reset) begin
        if (!Reset) begin
            Q <= 1'b0;
            Qn <= 1'b1;
        end else begin
            Q <= D;
            Qn <= ~D;
        end
    end
endmodule

// Módulo do Divisor de Clock Programável
module ClockDivider (
    output wire Clock_out,
    input wire Clock_in,
    input wire Reset,
    input wire [1:0] Sel
);

    wire d2, d4, d8, d16;          // Saídas dos flip-flops
    wire d2n, d4n, d8n, d16n;     // Saídas Inversas dos flip-flops

    // Instanciando D-flip-flops para o Ripple Counter
    d_flip_flop ff1 (.Q(d2), .Qn(d2n), .Clock(Clock_in),
```

```

        .Reset(Reset), .D(d2n));
d_flip_flop ff2 (.Q(d4), .Qn(d4n), .Clock(d2n), .Reset(Reset),
               .D(d4n));
d_flip_flop ff3 (.Q(d8), .Qn(d8n), .Clock(d4n), .Reset(Reset),
               .D(d8n));
d_flip_flop ff4 (.Q(d16), .Qn(d16n), .Clock(d8n), .Reset(Reset),
               .D(d16n));

// Instanciando o Multiplexador
assign Clock_out = (Sel == 2'b00) ? d2 :
                  (Sel == 2'b01) ? d4 :
                  (Sel == 2'b10) ? d8 : d16;
endmodule

```

CÓDIGO DO TESTBENCH:

```

`include "q5_ClockDivider.v"
`timescale 1ns/1ps

module ClockDivider_tb;

    // Entradas
    reg Clock_in;
    reg Reset;
    reg [1:0] Sel;

    // Saídas
    wire Clock_out;

    // Instanciar o módulo ClockDivider
    ClockDivider uut (
        .Clock_in(Clock_in),
        .Reset(Reset),
        .Sel(Sel),
        .Clock_out(Clock_out)
    );

    initial begin
        $dumpfile("q5_ClockDivider_tb.vcd");
    end

```

```

        $dumpvars(0, ClockDivider_tb);
    end

    // Monitorar as variáveis
    initial $monitor($time,
        " Clock_in = %b, Reset = %b, Sel = %b,
        Clock_out = %b",
        Clock_in, Reset, Sel, Clock_out);

    // Gerar Clock
    initial forever #5 Clock_in = ~Clock_in;

    // Testes
    initial begin
        Reset = 1'b0; // Ativar o Reset (nível baixo)
        Sel = 2'b00;
        Clock_in = 1'b0; // Inicializar o Clock

        #10 Reset = 1'b1; // Liberar o Reset (nível alto)

        // Testar diferentes seleções e esperar 16 ciclos de clock
        para cada um
            #20 Sel = 2'b01; #160;
            #20 Sel = 2'b10; #160;
            #20 Sel = 2'b11; #160;

        // Reativar o Reset
        #20 Reset = 1'b0; // Ativar o Reset novamente (nível baixo)

        // Finalizar a simulação
        #10 $finish;
    end

endmodule

```

OUTPUT:

```
danxc@danxc-popos-a72liv:~/Desktop/EEA25/Provas/P1$ iverilog q5_ClockDivider_tb.v
danxc@danxc-popos-a72liv:~/Desktop/EEA25/Provas/P1$ vvp a.out
VCD info: dumpfile q5_ClockDivider_tb.vcd opened for output.
 0 Clock_in = 0, Reset = 0, Sel = 00, Clock_out = 0
 5 Clock_in = 1, Reset = 0, Sel = 00, Clock_out = 0
10 Clock_in = 0, Reset = 1, Sel = 00, Clock_out = 0
15 Clock_in = 1, Reset = 1, Sel = 00, Clock_out = 1
20 Clock_in = 0, Reset = 1, Sel = 00, Clock_out = 1
25 Clock_in = 1, Reset = 1, Sel = 00, Clock_out = 0
30 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 1
35 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 1
40 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 1
45 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 0
50 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 0
55 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 0
60 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 0
65 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 1
70 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 1
75 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 1
80 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 1
85 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 0
90 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 0
95 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 0
100 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 0
105 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 1
110 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 1
115 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 1
120 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 1
125 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 0
130 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 0
135 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 0
140 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 0
145 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 1
150 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 1
155 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 1
160 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 1
165 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 0
170 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 0
175 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 0
180 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 0
185 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 1
190 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 1
195 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 1
200 Clock_in = 0, Reset = 1, Sel = 01, Clock_out = 1
205 Clock_in = 1, Reset = 1, Sel = 01, Clock_out = 0
210 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 1
215 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 1
220 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 1
225 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 1
230 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 1
235 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 1
240 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 1
245 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 0
250 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 0
255 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 0
260 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 0
265 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 0
270 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 0
275 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 0
280 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 0
285 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 1
290 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 1
295 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 1
```

```

300 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 1
305 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 1
310 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 1
315 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 1
320 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 1
325 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 0
330 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 0
335 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 0
340 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 0
345 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 0
350 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 0
355 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 0
360 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 0
365 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 1
370 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 1
375 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 1
380 Clock_in = 0, Reset = 1, Sel = 10, Clock_out = 1
385 Clock_in = 1, Reset = 1, Sel = 10, Clock_out = 1
390 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 0
395 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 0
400 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 0
405 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 1
410 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 1
415 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 1
420 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 1
425 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 1
430 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 1
435 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 1
440 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 1
445 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 1
450 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 1
455 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 1
460 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 1
465 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 1
470 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 1
475 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 1
480 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 1
485 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 0
490 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 0
495 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 0
500 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 0
505 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 0
510 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 0
515 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 0
520 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 0
525 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 0
530 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 0
535 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 0
540 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 0
545 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 0
550 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 0
555 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 0
560 Clock_in = 0, Reset = 1, Sel = 11, Clock_out = 0
565 Clock_in = 1, Reset = 1, Sel = 11, Clock_out = 1
570 Clock_in = 0, Reset = 0, Sel = 11, Clock_out = 0
575 Clock_in = 1, Reset = 0, Sel = 11, Clock_out = 0
580 Clock_in = 0, Reset = 0, Sel = 11, Clock_out = 0

```

SINAIS NO GTKWAVE:

